


EECS150

Section 1
Introduction to Combinational Logic
Fall 2001



2-Variable Logic Functions

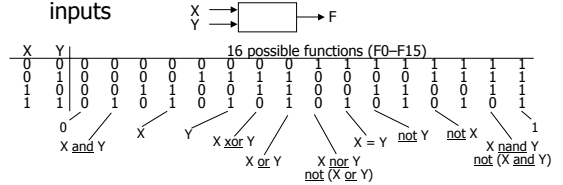- There are 16 possible functions of 2 input variables:
 - in general, there are 2^{2^n} functions of n inputs



Boolean algebra

- Boolean algebra
 - $B = \{0, 1\}$
 - $+$ is logical OR, \bullet is logical AND
 - ' is logical NOT
- All algebraic axioms hold

An algebraic structure

- An algebraic structure consists of
 - a set of elements B
 - binary operations $\{ +, \bullet \}$
 - and a unary operation $\{ ' \}$
 - such that the following axioms hold:
 - set B contains at least two elements, a, b , such that $a \neq b$
 - closure: $a + b$ is in B $a \bullet b$ is in B
 - commutativity: $a + b = b + a$ $a \bullet b = b \bullet a$
 - associativity: $a + (b + c) = (a + b) + c$ $a \bullet (b \bullet c) = (a \bullet b) \bullet c$
 - identity: $a + 0 = a$ $a \bullet 1 = a$
 - distributivity: $a + (b \bullet c) = (a + b) \bullet (a + c)$ $a \bullet (b + c) = (a \bullet b) + (a \bullet c)$
 - complementarity: $a + a' = 1$ $a \bullet a' = 0$

Axioms and Theorems

- Identity
 - $X + 0 = X$ 1D. $X \bullet 1 = X$
- Null
 - $X + 1 = 1$ 2D. $X \bullet 0 = 0$
- Idempotency:
 - $X + X = X$ 3D. $X \bullet X = X$
- Involution:
 - $(X')' = X$
- Complementarity:
 - $X + X' = 1$ 5D. $X \bullet X' = 0$
- Commutativity:
 - $X + Y = Y + X$ 6D. $X \bullet Y = Y \bullet X$
- Associativity:
 - $(X + Y) + Z = X + (Y + Z)$ 7D. $(X \bullet Y) \bullet Z = X \bullet (Y \bullet Z)$

Axioms and theorems

- Distributivity:
 - $X \bullet (Y + Z) = (X \bullet Y) + (X \bullet Z)$ 8D. $X + (Y \bullet Z) = (X + Y) \bullet (X + Z)$
- Uniting:
 - $X \bullet Y + X \bullet Y' = X$ 9D. $(X + Y) \bullet (X + Y') = X$
- Absorption:
 - $X + X \bullet Y = X$ 10D. $X \bullet (X + Y) = X$
 - $(X + Y') \bullet Y = X \bullet Y$ 11D. $(X \bullet Y') + Y = X + Y$
- Factoring:
 - $(X + Y) \bullet (X' + Z) = X \bullet Z + X' \bullet Y$ 12D. $X \bullet Y + X' \bullet Z = (X + Z) \bullet (X' + Y)$
- Consensus:
 - $(X \bullet Y) + (Y \bullet Z) + (X' \bullet Z) = X \bullet Y + X' \bullet Z$ 13D. $(X + Y) \bullet (Y + Z) \bullet (X' + Z) = (X + Y) \bullet (X' + Z)$

Axioms and theorems

- de Morgan's:
 - 14. $(X + Y + \dots)' = X' \cdot Y' \cdot \dots$ 14D. $(X \cdot Y \cdot \dots)' = X' + Y' + \dots$
- generalized de Morgan's:
 - 15. $f(X_1, X_2, \dots, X_n, 0, 1, +, \cdot) = f(X_1', X_2', \dots, X_n', 1, 0, \cdot, +)$
- establishes relationship between \cdot and $+$

A	B	F	\bar{A}	\bar{B}	$\bar{A} + \bar{B}$	\bar{F}	$\overline{A + B}$
0	0	0	1	1	1	1	0
0	1	0	1	0	1	1	0
1	0	0	0	1	1	1	0
1	1	1	0	0	0	0	1

EECS150 - Fall 2001

1-7

Axioms and theorems

- Duality
 - Dual of a Boolean expression is derived by replacing \cdot by $+$, $+$ by \cdot , 0 by 1, and 1 by 0, and leaving variables unchanged
 - Any theorem that can be proven is thus also proven for its dual!
 - Meta-theorem (a theorem about theorems)
- duality:
 - 16. $X + Y + \dots \Leftrightarrow X \cdot Y \cdot \dots$
- generalized duality:
 - 17. $f(X_1, X_2, \dots, X_n, 0, 1, +, \cdot) \Leftrightarrow f(X_1, X_2, \dots, X_n, 1, 0, \cdot, +)$
- Different than deMorgan's Law
 - this is a statement about theorems
 - this is not a way to manipulate (re-write) expressions

EECS150 - Fall 2001

1-8

Proving theorems (rewriting)

- Using the axioms of Boolean algebra:
 - e.g., prove the theorem: $X \cdot Y + X \cdot Y' = X$

$$\begin{array}{l} \text{distributivity (8)} \\ \text{complementarity (5)} \\ \text{identity (1D)} \end{array} \quad \begin{array}{l} X \cdot Y + X \cdot Y' = X \cdot (Y + Y') \\ X \cdot (Y + Y') = X \cdot (1) \\ X \cdot (1) = X \checkmark \end{array}$$

- e.g., prove the theorem: $X + X \cdot Y = X$

$$\begin{array}{l} \text{identity (1D)} \\ \text{distributivity (8)} \\ \text{identity (2)} \\ \text{identity (1D)} \end{array} \quad \begin{array}{l} X + X \cdot Y = X \cdot 1 + X \cdot Y \\ X \cdot 1 + X \cdot Y = X \cdot (1 + Y) \\ X \cdot (1 + Y) = X \cdot (1) \\ X \cdot (1) = X \checkmark \end{array}$$

EECS150 - Fall 2001

1-9

Proving theorems (perfect induction)

- Using perfect induction (complete truth table):

- e.g., de Morgan's:

$$\begin{array}{l} (X + Y)' = X' \cdot Y' \\ \text{NOR is equivalent to AND} \\ \text{with inputs complemented} \end{array} \quad \begin{array}{c|c|c|c|c|c} X & Y & X' & Y' & (X + Y)' & X' \cdot Y' \\ \hline 0 & 0 & 1 & 1 & 1 & 1 \\ 0 & 1 & 1 & 0 & 0 & 0 \\ 1 & 0 & 0 & 1 & 0 & 0 \\ 1 & 1 & 0 & 0 & 0 & 0 \end{array}$$

$$\begin{array}{l} (X \cdot Y)' = X' + Y' \\ \text{NAND is equivalent to OR} \\ \text{with inputs complemented} \end{array} \quad \begin{array}{c|c|c|c|c|c} X & Y & X' & Y' & (X \cdot Y)' & X' + Y' \\ \hline 0 & 0 & 1 & 1 & 1 & 1 \\ 0 & 1 & 1 & 0 & 1 & 1 \\ 1 & 0 & 0 & 1 & 1 & 1 \\ 1 & 1 & 0 & 0 & 0 & 0 \end{array}$$

EECS150 - Fall 2001

1-10

Logic Functions

- Any logic function that can be expressed as a truth table can be written as an expression in Boolean algebra using the operators: $'$, $+$, and \cdot

X	Y	$X \cdot Y$	X	Y	X'	$X' \cdot Y'$
0	0	0	0	0	1	0
0	1	0	0	1	1	1
1	0	0	1	0	0	0
1	1	1	1	1	0	0

X	Y	X'	Y'	$X \cdot Y$	$X' \cdot Y'$	$(X \cdot Y) + (X' \cdot Y')$
0	0	1	1	0	1	1
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	1	0	0	1	0	1

$$(X \cdot Y) + (X' \cdot Y') = X = Y$$

Boolean expression that is true when the variables X and Y have the same value and false, otherwise

X, Y are Boolean algebra variables

EECS150 - Fall 2001

1-11

Cost of different logic functions

- Different functions are easier or harder to implement
 - Each has a cost associated with the number of switches needed
 - 0 (F0) and 1 (F15): require 0 switches, directly connect output to low/high
 - X (F3) and Y (F5): require 0 switches, output is one of inputs
 - X' (F12) and Y' (F10): require 2 switches for "inverter" or NOT-gate
 - X nor Y (F4) and X nand Y (F14): require 4 switches
 - X or Y (F7) and X and Y (F1): require 6 switches
 - X = Y (F9) and X \oplus Y (F6): require 16 switches
- Because NOT, NOR, and NAND are the cheapest they are the functions we implement the most in practice

EECS150 - Fall 2001

1-12

A simple example

- 1-bit binary adder
 - inputs: A, B, Carry-in
 - outputs: Sum, Carry-out



A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$S = A' B' Cin + A' B Cin' + A B' Cin' + A B Cin$$

$$Cout = A' B Cin + A B' Cin + A B Cin' + A B Cin$$


Apply theorems to simplify

- The theorems of Boolean algebra can simplify Boolean expressions
 - e.g., full adder's carry-out function (same rules apply to any function)

$$\begin{aligned}
 Cout &= A' B Cin + A B' Cin + A B Cin' + A B Cin \\
 &= A' B Cin + A B' Cin + A B Cin' + A B Cin + A B Cin \\
 &= A' B Cin + A B Cin + A B' Cin + A B Cin' + A B Cin \\
 &= (A' + A) B Cin + A B' Cin + A B Cin' + A B Cin \\
 &= (1) B Cin + A B' Cin + A B Cin' + A B Cin \\
 &= B Cin + A B' Cin + A B Cin' + A B Cin + A B Cin \\
 &= B Cin + A B' Cin + A B Cin + A B Cin' + A B Cin \\
 &= B Cin + A (B' + B) Cin + A B Cin' + A B Cin \\
 &= B Cin + A (1) Cin + A B Cin' + A B Cin \\
 &= B Cin + A Cin + A B (Cin' + Cin) \\
 &= B Cin + A Cin + A B (1) \\
 &= B Cin + A Cin + A B
 \end{aligned}$$

From expressions to logic gates

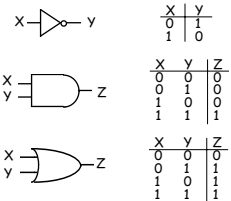- NOT $X' \quad X \quad \sim X$
- AND $X \cdot Y \quad XY \quad X \wedge Y$
- OR $X + Y \quad X \vee Y$



From expressions to logic gates

- NAND $X, Y \rightarrow Z$
- NOR $X, Y \rightarrow Z$
- XOR $X \oplus Y \rightarrow Z$
- XNOR $X = Y \rightarrow Z$

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	1

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	1

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	0


X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	1

$X \text{ xor } Y = X Y' + X' Y$
X or Y but not both
("inequality", "difference")

$X \text{ xnor } Y = X Y + X' Y'$
X and Y are the same
("equality", "coincidence")


From expressions to logic gates

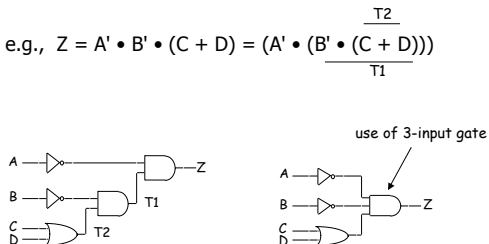- More than one way to map expressions to gates
 - e.g., $Z = A' \cdot B' \cdot (C + D) = (A' \cdot (B' \cdot (C + D)))$




Waveform view of logic functions

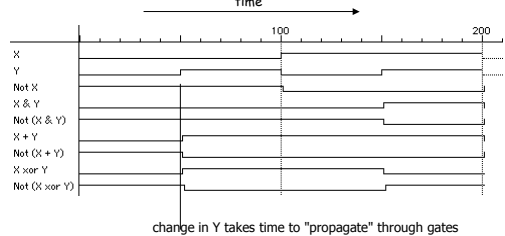- Just a sideways truth table
 - but note how edges don't line up exactly
 - it takes time for a gate to switch its output!



Different realizations of a function

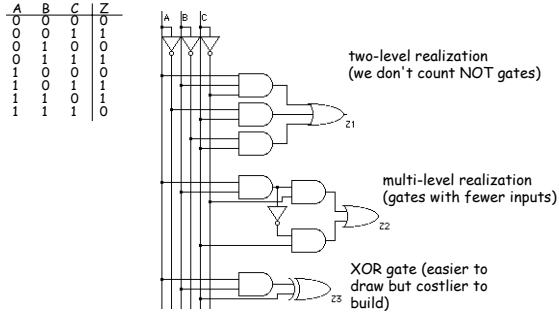

EECS150 - Fall 2001

1-19

Which realization is best?

- Reduce number of inputs
 - literal: input variable (complemented or not)
 - can approximate cost of logic gate as 2 transistors per literal
 - why not count inverters?
 - Fewer literals means less transistors
 - smaller circuits
 - Fewer inputs implies faster gates
 - gates are smaller and thus also faster
 - Fan-ins (# of gate inputs) are limited in some technologies
- Reduce number of gates
 - Fewer gates (and the packages they come in) means smaller circuits
 - directly influences manufacturing costs

EECS150 - Fall 2001

1-20

Which is the best realization?


- Reduce number of levels of gates
 - Fewer level of gates implies reduced signal propagation delays
 - Minimum delay configuration typically requires more gates
 - wider, less deep circuits
- How do we explore tradeoffs between increased circuit delay and size?
 - Automated tools to generate different solutions
 - Logic minimization: reduce number of gates and complexity
 - Logic optimization: reduction while trading off against delay

EECS150 - Fall 2001

1-21

Are all realizations equivalent?

- Under the same input stimuli, the three alternative implementations have almost the same waveform behavior
 - delays are different
 - glitches (hazards) may arise
 - variations due to differences in depth, structure

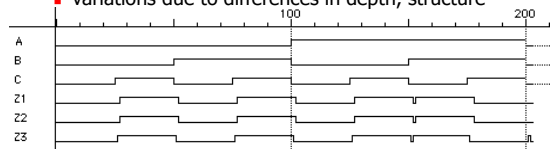


EECS150 - Fall 2001

1-22

Timing

- Two key concepts: what {0,1} and when (timing)
 - How fast can I move or process information?
 - Fundamental limitations:
 - speed of light: 3×10^8 m/sec vacuum
 - $\sim 2 \times 10^8$ m/sec conduction
 - switching time: capacitance & inductance


Zeroth order model

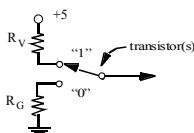

EECS150 - Fall 2001

1-23

Voltage model (more physical)

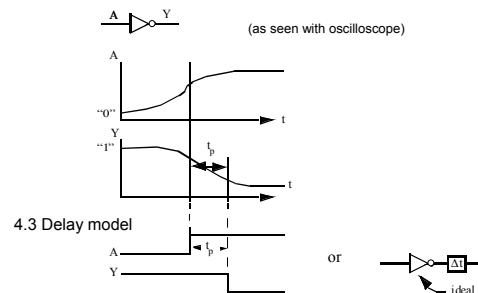

EECS150 - Fall 2001

1-24


Timing

- Why big deal?
- Dynamic output \neq static output ("glitches")

Example: XOR function implemented from AND, OR, INV

idealization: unit delay in each symbol


$$Y = A \cdot \bar{B} + \bar{A} \cdot B$$

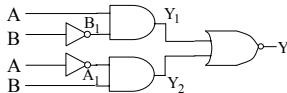

EECS150 - Fall 2001

1-25

Timing Diagram

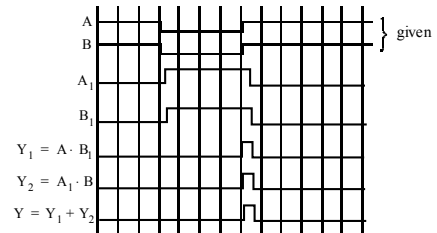

Static behavior fine $1 \oplus 1 = 0, 0 \oplus 0 = 0 \checkmark$

Dynamic behavior **glitch** \rightarrow fundamental feature of switching

EECS150 - Fall 2001

1-26

Implementing Boolean functions

- Technology independent
 - Canonical forms
 - Two-level forms
 - Multi-level forms
- Technology choices
 - Packages of a few gates
 - Regular logic
 - Two-level programmable logic
 - Multi-level programmable logic

EECS150 - Fall 2001

1-27

Canonical forms

- Truth table is the unique signature of a Boolean function
- Many alternative gate realizations may have the same truth table
- Canonical forms
 - Standard forms for a Boolean expression
 - Provides a unique algebraic signature

EECS150 - Fall 2001

1-28

Sum-of-products canonical forms

- Also known as disjunctive normal form
- Also known as minterm expansion

A	B	C	F	F'
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	0	1

$F = 001 \ 011 \ 101 \ 110 \ 111$
 $F = A'B'C + A'BC + AB'C + ABC + ABC$
 $F' = A'B'C' + A'BC' + AB'C'$

EECS150 - Fall 2001

1-29

Sum-of-products canonical form

- Product term (or minterm)
 - ANDed product of literals – input combination for which output is true
 - Each variable appears exactly once, in true or inverted form (but not both)

A	B	C	minterms
0	0	0	A'B'C' m0
0	0	1	A'B'C m1
0	1	0	A'BC' m2
0	1	1	A'BC m3
1	0	0	AB'C' m4
1	0	1	AB'C m5
1	1	0	ABC' m6
1	1	1	ABC m7

F in canonical form:
 $F(A, B, C) = \Sigma m(1, 3, 5, 6, 7)$
 $= m1 + m3 + m5 + m6 + m7$
 $= A'B'C + A'BC + AB'C + ABC + ABC$

canonical form \neq minimal form
 $F(A, B, C) = A'B'C + A'BC + AB'C + ABC + ABC$
 $= (A'B' + A'B + AB' + AB)C + ABC$
 $= (A' + A)(B' + B)C + ABC$
 $= C + ABC$
 $= ABC' + C$
 $= AB + C$

short-hand notation for minterms of 3 variables

EECS150 - Fall 2001

1-30

Product-of-sums canonical form

- Also known as conjunctive normal form
- Also known as maxterm expansion

$F = 000$ 010 100
 $F = (A+B+C) (A+B'+C) (A'+B+C)$

A	B	C	F	F'
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

$F' = (A + B + C) (A + B' + C') (A' + B + C) (A' + B' + C) (A' + B' + C)$

EECS150 - Fall 2001

1-31

Product-of-sums canonical form

- Sum term (or maxterm)
 - ORed sum of literals – input combination for which output is false
 - each variable appears exactly once, in true or inverted form (but not both)

A	B	C	maxterms
0	0	0	A+B+C M0
0	0	1	A+B+C' M1
0	1	0	A+B'+C M2
0	1	1	A+B'+C' M3
1	0	0	A'+B+C M4
1	0	1	A'+B+C' M5
1	1	0	A'+B'+C M6
1	1	1	A'+B'+C' M7

F in canonical form:
 $F(A, B, C) = \Pi M(0,2,4)$
 $= M0 \cdot M2 \cdot M4$
 $= (A + B + C) (A + B' + C) (A' + B + C)$

canonical form ≠ minimal form
 $F(A, B, C) = (A + B + C) (A + B' + C) (A' + B + C)$
 $= (A + B + C) (A + B' + C)$
 $= (A + B + C) (A' + B + C)$
 $= (A + C) (B + C)$

short-hand notation for maxterms of 3 variables

EECS150 - Fall 2001

1-32


Relating S-o-P & P-o-S

- Sum-of-products
 - $F' = A'B'C' + A'BC' + AB'C'$
- Apply de Morgan's
 - $(F')' = (A'B'C' + A'BC' + AB'C')'$
 - $F = (A + B + C) (A + B' + C) (A' + B + C)$
- Product-of-sums
 - $F' = (A + B + C) (A + B' + C) (A' + B + C) (A' + B' + C) (A' + B' + C)$
- Apply de Morgan's
 - $(F')' = ((A + B + C)(A + B' + C)(A' + B + C)(A' + B' + C)(A' + B' + C))'$
 - $F = A'B'C' + A'BC' + AB'C' + ABC' + ABC$

EECS150 - Fall 2001

1-33

Example: $F = AB + C$

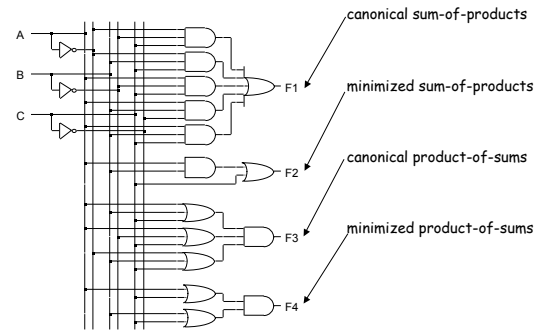


EECS150 - Fall 2001

1-34

Waveforms

- Waveforms are essentially identical
 - Except for timing hazards (glitches)
 - Delays almost identical (modeled as a delay per level, not type of gate or number of inputs to gate)

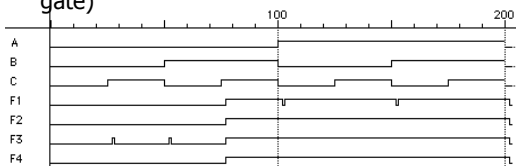

EECS150 - Fall 2001

1-35

Mapping

- Minterm to maxterm conversion
 - Use maxterms whose indices do not appear in minterm expansion
 - e.g., $F(A,B,C) = \Sigma m(1,3,5,6,7) = \Pi M(0,2,4)$
- Maxterm to minterm conversion
 - Use minterms whose indices do not appear in maxterm expansion
 - e.g., $F(A,B,C) = \Pi M(0,2,4) = \Sigma m(1,3,5,6,7)$
- Minterm expansion of F to minterm expansion of F'
 - Use minterms whose indices do not appear
 - e.g., $F(A,B,C) = \Sigma m(1,3,5,6,7)$ $F'(A,B,C) = \Sigma m(0,2,4)$
- Maxterm expansion of F to maxterm expansion of F'
 - Use maxterms whose indices do not appear
 - e.g., $F(A,B,C) = \Pi M(0,2,4)$ $F'(A,B,C) = \Pi M(1,3,5,6,7)$

EECS150 - Fall 2001

1-36

Incompletely specified functions

- Example: binary coded decimal increment by 1
 - BCD digits encode decimal digits 0 – 9 in bit patterns 0000 – 1001

A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1
0	0	0	1	0	1	1	0
0	0	1	0	0	1	1	1
0	0	1	1	1	0	0	1
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	1	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	0	0	0	1
1	0	0	1	0	0	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

off-set of W
 on-set of W
 don't care (DC) set of W
 these inputs patterns should never be encountered in practice - "don't care" about associated output values, can be exploited in minimization

EECS150 - Fall 2001

1-37

Notation

- Don't cares and canonical forms
 - So far, only represented on-set
 - Also represent don't-care-set
 - Need two of the three sets (on-set, off-set, dc-set)
- Canonical representations of the BCD increment by 1 function:
 - $Z = m_0 + m_2 + m_4 + m_6 + m_8 + d_{10} + d_{11} + d_{12} + d_{13} + d_{14} + d_{15}$
 - $Z = \Sigma [m(0,2,4,6,8) + d(10,11,12,13,14,15)]$
 - $Z = M_1 \cdot M_3 \cdot M_5 \cdot M_7 \cdot M_9 \cdot D_{10} \cdot D_{11} \cdot D_{12} \cdot D_{13} \cdot D_{14} \cdot D_{15}$
 - $Z = \Pi [M(1,3,5,7,9) \cdot D(10,11,12,13,14,15)]$

EECS150 - Fall 2001

1-38