

EECS150

Section 3

Field-Programmable Gate Arrays

Fall 2001




From design to product

- Specification of design constraints/goals
- Investigation of concepts/feasibility
- Logic design
- Verification
- Static timing analysis
- Tape Release
- Implementation
- Electrical Debug
- Ship the part!

Programmable Logic

- Use a single chip (or a small number of chips)
- Program it for the circuit you want
- No reason for the circuit to be small

Programmable Logic Technologies


- Fuse and anti-fuse
 - Fuse makes or breaks link between two wires 
 - Typical connections are 50-300 ohm
 - One-time programmable (testing before programming?)
 - Very high density
- EPROM and EEPROM
 - High power consumption
 - Typical connections are 2K-4K ohm
 - Fairly high density
- RAM-based
 - Memory bit controls a switch that connects/disconnects two wires
 - Typical connections are .5K-1K ohm
 - Can be programmed and re-programmed *in the circuit*
 - Low density

Field-Programmable Gate Arrays

- PALs, PLAs = 10 - 100 Gate Equivalents
- Field Programmable Gate Arrays = FPGAs
 - Altera MAX Family
 - Actel Programmable Gate Array
 - Xilinx Logical Cell Array
- 100 - 1000(s) of Gate Equivalents!

Field-Programmable Gate Arrays

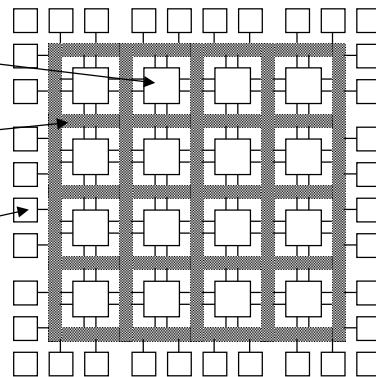- Logic blocks
 - To implement combinational and sequential logic
- Interconnect
 - Wires to connect inputs and outputs to logic blocks
- I/O blocks
 - Special logic blocks at periphery of device for external connections
- Key questions:
 - How to make logic blocks programmable?
 - How to connect the wires?
 - *After the chip has been fabricated?*




Tradeoffs in FPGAs


- Logic block - how are functions implemented: fixed functions (manipulate inputs) or programmable?
 - Support complex functions, need fewer blocks, but they are bigger so less of them on chip
 - Support simple functions, need more blocks, but they are smaller so more of them on chip
- Interconnect
 - How are logic blocks arranged?
 - How many wires will be needed between them?
 - Are wires evenly distributed across chip?
 - Programmability slows wires down – are some wires specialized to long distances?
 - How many inputs/outputs must be routed to/from each logic block?
 - What utilization are we willing to accept? 50%? 20%? 90%?

Xilinx Programmable Gate Arrays

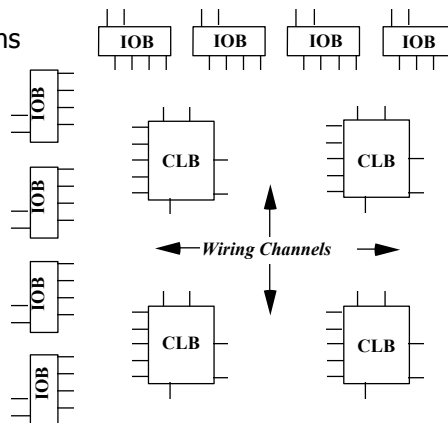- CLB - Configurable Logic Block
 - 5-input, 1 output function
 - or 2 4-input, 1 output functions
 - optional register on outputs
- Built-in fast carry logic
- Can be used as memory
- Three types of routing
 - direct
 - general-purpose
 - long lines of various lengths
- RAM-programmable
 - can be reconfigured



The Xilinx 4000 CLB

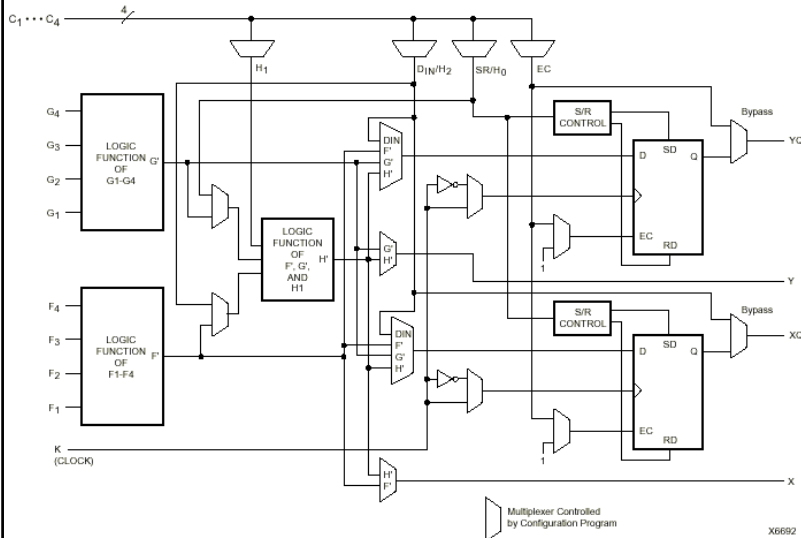

Two 4-in functions, registered out

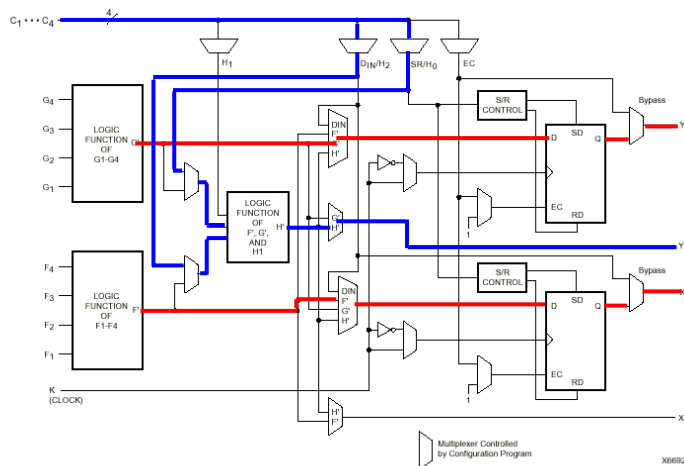


Figure 1: Simplified Block Diagram of XC4000 Series CLB (RAM and Carry Logic functions not shown)

5-in function, combinational out

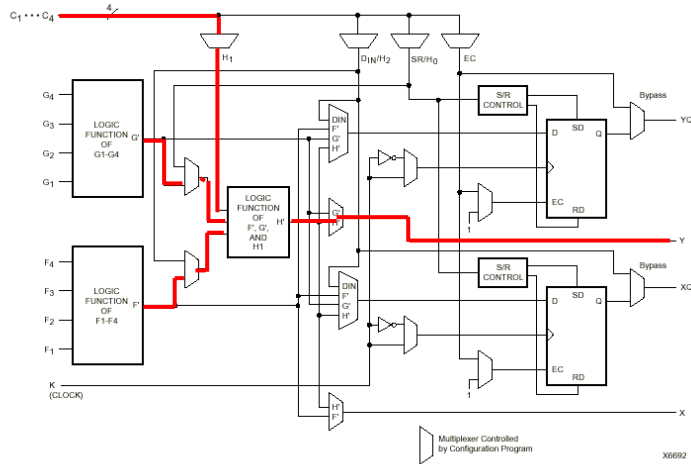


Figure 1: Simplified Block Diagram of XC4000 Series CLB (RAM and Carry Logic functions not shown)

Xilinx 4000 Interconnect

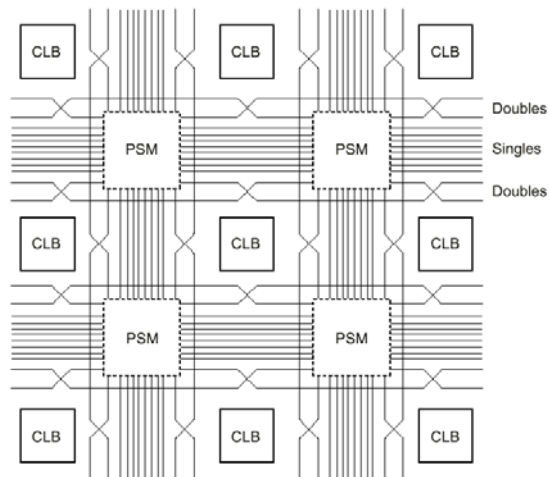


Figure 28: Single- and Double-Length Lines, with Programmable Switch Matrices (PSMs)

Switch Matrix



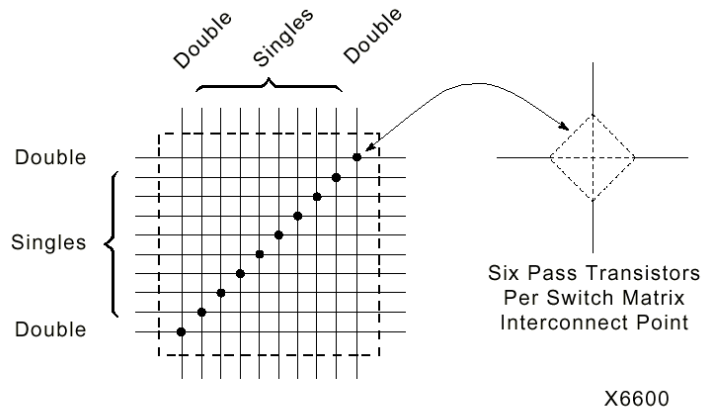


Figure 26: Programmable Switch Matrix (PSM)

Xilinx 4000 Interconnect Details

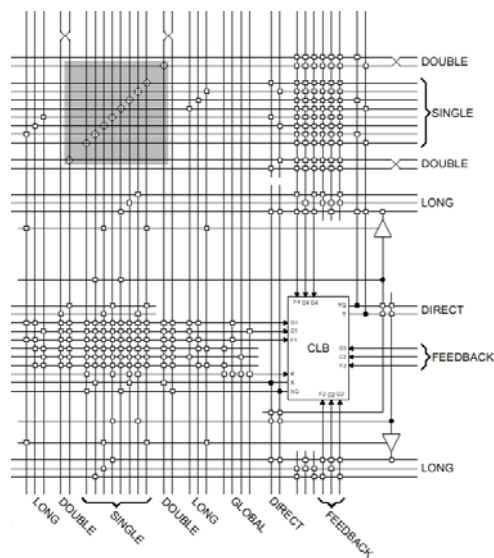


Xilinx 4000 IOB

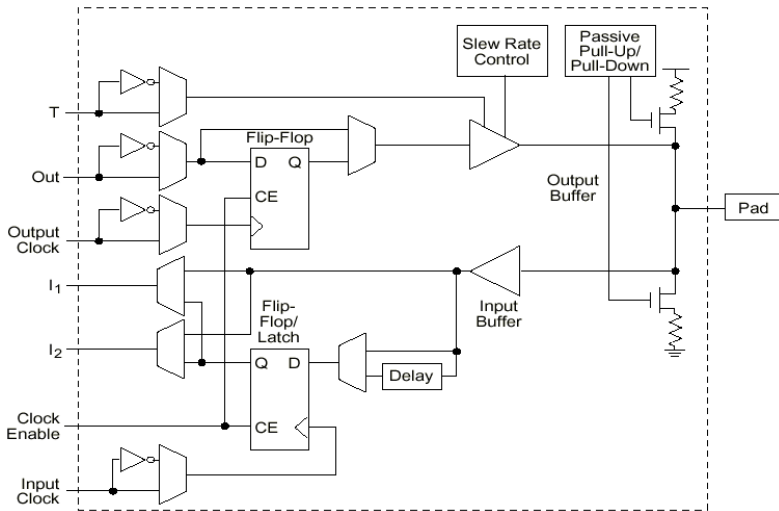

Combinational Logic Examples

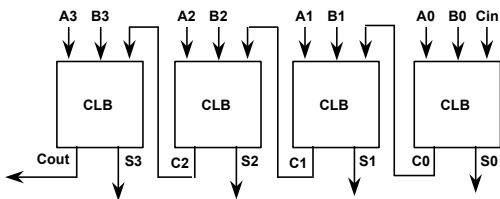- Key: General functions are generally limited to 5 inputs
 - (4 even better - 1/2 CLB)
 - *No limitation on function complexity*
- Example
 - 2-bit comparator:
 - A B = C D and A B > C D implemented with 1 CLB
 - (GT) $F = A C' + A B D' + B C' D'$
 - (EQ) $G = A'B'C'D' + A'B C'D + A B' C D' + A B C D$
 - 4-bit binary adder:



Computer-Aided Design

- Can't design FPGAs by hand
 - Way too much logic to manage, hard to make changes
- Hardware description languages
 - Specify functionality of logic at a high level
- Validation: high-level simulation to catch specification errors
 - Verify pin-outs and connections to other system components
 - Low-level to verify mapping and check performance
- Logic synthesis
 - Process of compiling HDL program into logic gates and flip-flops
- Technology mapping
 - Map the logic onto elements available in the implementation technology (LUTs for Xilinx FPGAs)

CAD Tool Path (cont'd)

- Placement and routing
 - Assign logic blocks to functions
 - Make wiring connections
- Timing analysis - verify paths
 - Determine delays as routed
 - Look at critical paths and ways to improve
- Partitioning and constraining
 - If design does not fit or is unroutable as placed split into multiple chips
 - If design is too slow prioritize critical paths, fix placement of cells, etc.
 - Few tools to help with these tasks exist today
- Generate programming files - bits to be loaded into chip for configuration

Xilinx CAD Tools

- Verilog (or VHDL) use to specify logic at a high-level
 - Combine with schematics, library components
- Synopsys
 - Compiles Verilog to logic
 - Maps logic to the FPGA cells
 - Optimizes logic
- Xilinx APR - automatic place and route (simulated annealing)
 - Provides controllability through constraints
 - Handles global signals
- Xilinx Xdelay - measure delay properties of mapping and aid in iteration
- Xilinx XACT - design editor to view final mapping results