

EECS150

Section 7

Finite State Machine Case Studies

Fall 2001



General FSM Design Procedure

- (1) Determine inputs and outputs
- (2) Determine possible states of machine
 - State minimization
- (3) Encode states and outputs into a binary code
 - State assignment or state encoding
 - Output encoding
 - Possibly input encoding (if under our control)
- (4) Realize logic to implement functions for states and outputs
 - Combinational logic implementation and optimization
 - Choices in steps 2 and 3 have large effect on resulting logic

Finite String Pattern Recognizer


- Finite String Pattern Recognizer
 - One input (X) and one output (Z)
 - Output is asserted whenever the input sequence ...010... has been observed, as long as the sequence 100 has never been seen
- Step 1: Understanding the Problem Statement
 - Sample input/output behavior:

X: 0 0 1 0 1 0 1 0 0 1 0 ...
Z: 0 0 0 1 0 1 0 1 0 0 0 ...

X: 1 1 0 1 1 0 1 0 0 1 0 ...
Z: 0 0 0 0 0 0 0 1 0 0 0 ...

Finite String Pattern Recognizer

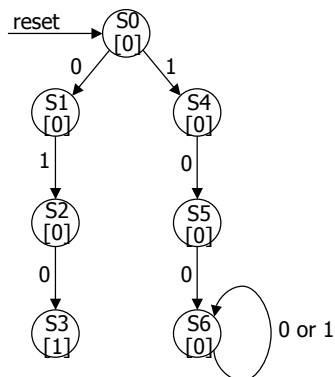- Step 2: Draw State Diagram
 - For the strings that must be recognized, i.e., 010 and 100
 - Moore implementation




Finite String Pattern Recognizer

- Exit conditions from state S3: have recognized ...010
 - If next input is 0 then have ...0100 = ...100 (state S6)
 - If next input is 1 then have ...0101 = ...01 (state S2)


Exit conditions from S1:
recognizes strings of form ...0
(no 1 seen);
loop back to S1 if input is 0

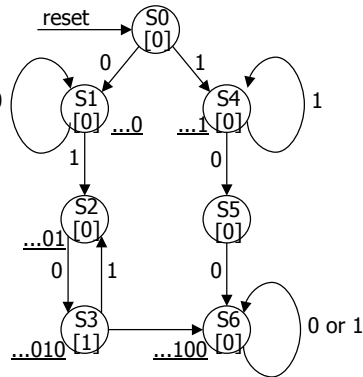Exit conditions from S4:
recognizes strings of form ...1
(no 0 seen);
loop back to S4 if input is 1



Finite String Pattern Recognizer

- S2 and S5 still have incomplete transitions
 - S2 = ...01; If next input is 1, then string could be prefix of (01)1(00) S4 handles just this case
 - S5 = ...10; If next input is 1, then string could be prefix of (10)1(0) S2 handles just this case
- Reuse states as much as possible
 - Look for same meaning
 - State minimization leads to smaller number of bits to represent states
- Once all states have complete set of transitions we have final state diagram

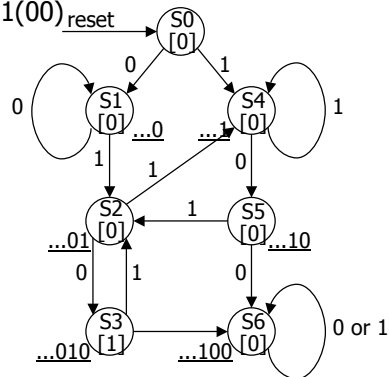


Complex Counter

- Synchronous 3-bit counter has a mode control M
 - When M = 0, the counter counts up in the binary sequence
 - When M = 1, the counter advances through the Gray code sequence
 - binary: 000, 001, 010, 011, 100, 101, 110, 111
 - Gray: 000, 001, 011, 010, 110, 111, 101, 100
- Valid I/O behavior (partial)

Mode Input M	Current State	Next State
0	000	001
0	001	010
1	010	110
1	110	111
1	111	101
0	101	110
0	110	111


Complex Counter

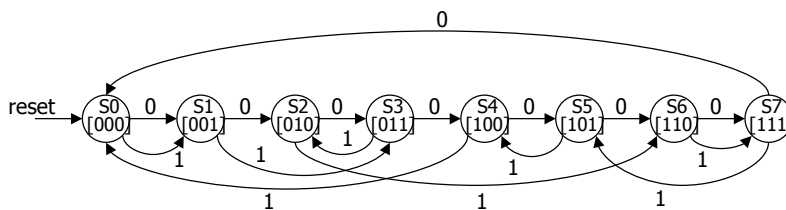- Deriving State Diagram
 - One state for each output combination
 - Add appropriate arcs for the mode control



Datapath and Control

- Digital hardware systems = data-path + control
 - Datapath: registers, counters, combinational functional units (e.g., ALU), communication (e.g., busses)
 - Control: FSM generating sequences of control signals that instructs datapath what to do next

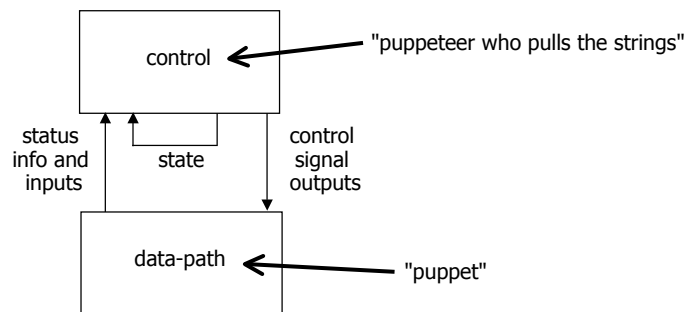

EECS150 - Fall 2001

1-9

Digital Combinational Lock

- Door Combination Lock:
 - Punch in 3 values in sequence and the door opens; if there is an error the lock must be reset; once the door opens the lock must be reset
 - Inputs: sequence of input values, reset
 - Outputs: door open/close
 - Memory: must remember combination or always have it available
 - Open questions: how do you set the internal combination?
 - Stored in registers (how loaded?)
 - Hardwired via switches set by user

EECS150 - Fall 2001

1-10

Implementation in Software

```
integer combination_lock ( ) {
    integer v1, v2, v3;
    integer error = 0;
    static integer c[3] = 3, 4, 2;

    while (!new_value( ));
    v1 = read_value( );
    if (v1 != c[1]) then error = 1;


    while (!new_value( ));
    v2 = read_value( );
    if (v2 != c[2]) then error = 1;

    while (!new_value( ));
    v3 = read_value( );
    if (v2 != c[3]) then error = 1;

    if (error == 1) then return(0); else return (1);
}
```


Specification

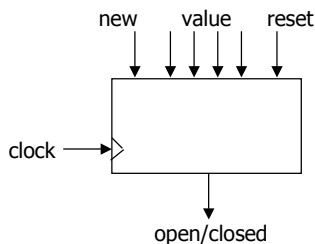- How many bits per input value?
- How many values in sequence?
- How do we know a new input value is entered?
- What are the states and state transitions of the system?




State Diagram

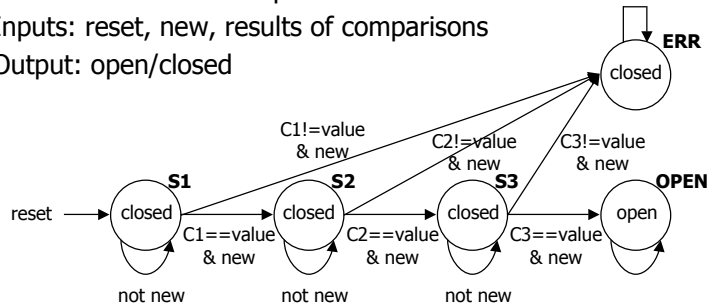- States: 5 states
 - Represent point in execution of machine
 - Each state has outputs
- Transitions: 6 from state to state, 5 self transitions, 1 global
 - Changes of state occur when clock says its ok
 - Based on value of inputs
- Inputs: reset, new, results of comparisons
- Output: open/closed



Datapath and Control Structure

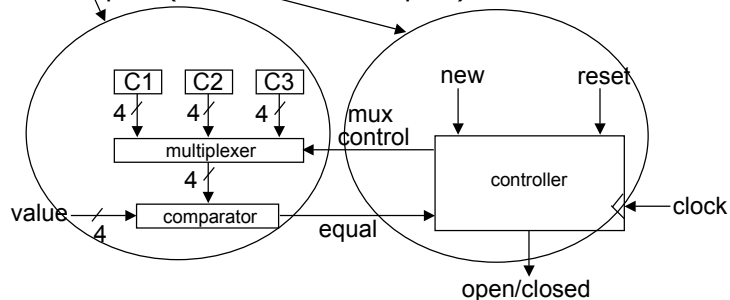- Datapath
 - Storage registers for combination values
 - Multiplexer
 - Comparator
- Control
 - Finite-state machine controller
 - Control for data-path (which value to compare)



State Table for Combination Lock

■ Finite-State Machine


- Refine state diagram to take internal structure into account
- State table ready for encoding

reset	new	equal	state	next state	mux	open/closed
1	-	-	-	S1	C1	closed
0	0	-	S1	S1	C1	closed
0	1	0	S1	ERR	-	closed
0	1	1	S1	S2	C2	closed
...						
0	1	1	S3	OPEN	-	open
...						

Encodings for Combination Lock

■ Encode state table

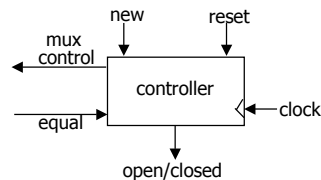- State can be: S1, S2, S3, OPEN, or ERR
 - Needs at least 3 bits to encode: 000, 001, 010, 011, 100
 - And as many as 5: 00001, 00010, 00100, 01000, 10000
 - Choose 4 bits: 0001, 0010, 0100, 1000, 0000
- Output mux can be: C1, C2, or C3
 - Needs 2 to 3 bits to encode
 - Choose 3 bits: 001, 010, 100
- Output open/closed can be: open or closed
 - Needs 1 or 2 bits to encode
 - Choose 1 bit: 1, 0




reset	new	equal	state	next state	mux	open/closed
1	-	-	-	0001	001	0
0	0	-	0001	0001	001	0
0	1	0	0001	0000	-	0
0	1	1	0001	0010	010	0
...						
0	1	1	0100	1000	-	1
...						

EECS150 - Fall 2001

mux is identical to last 3 bits of state
open/closed is identical to first bit of state therefore, we do not even need to implement FFs to hold state, just use outputs

Datapath Implementation

- Multiplexer
 - Easy to implement as combinational logic when few inputs
 - Logic can easily get too big for most PLDs

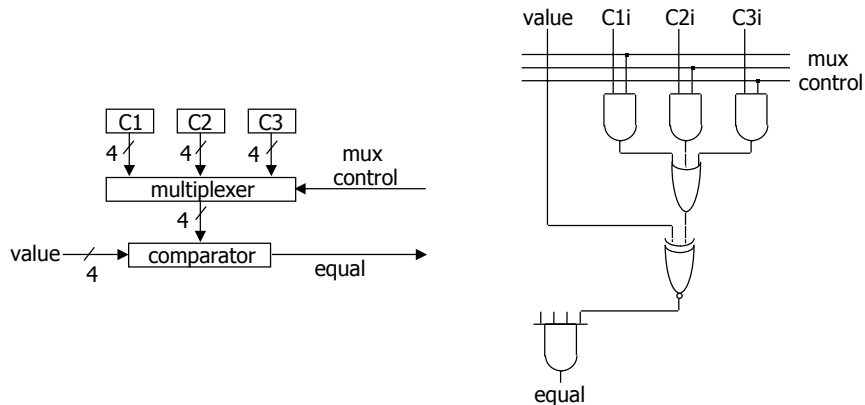


EECS150 - Fall 2001

1-17

Datapath Implementation

- Tri-State Logic
 - Utilize a third output state: "no connection" or "float"
 - Connect outputs together as long as only one is "enabled"
 - Open-collector gates can only output 0, not 1
 - Can be used to implement logical AND with only wires


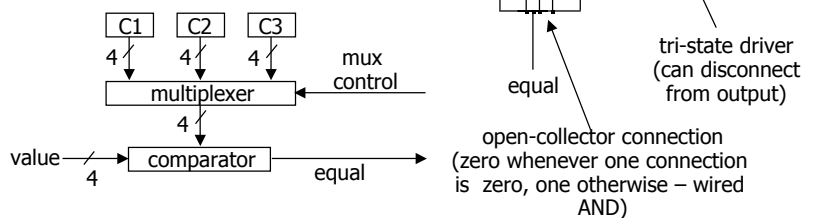


EECS150 - Fall 2001

1-18


Tri-State Gates

- Third value
 - Logic values: "0", "1"
 - Don't care: "X" (must be 0 or 1 in real circuit!)
 - Third value or state: "Z" — high impedance, infinite R, no connection
- Tri-state gates
 - Additional input – output enable (OE)
 - Output values are 0, 1, and Z
 - When OE is high, the gate functions normally
 - When OE is low, the gate is disconnected from wire at output
 - Allows more than one gate to be connected to the same output wire
 - As long as only one has its output enabled at any one time (otherwise, sparks could fly)

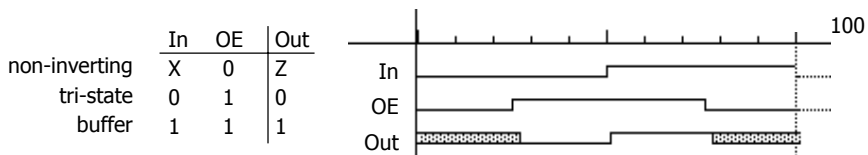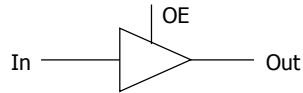

Tri-State and Multiplexing

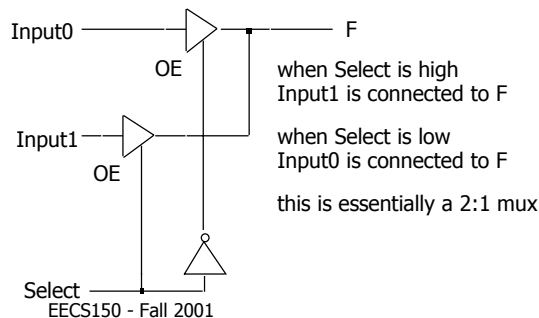- When Using Tri-State Logic
 - (1) Never more than one "driver" for a wire at any one time (pulling high and low at same time can severely damage circuits)
 - (2) Only use value on wire when its being driven (using a floating value may cause failures)
- Using Tri-State Gates to Implement an Economical Multiplexer



Digital Lock (New Datapath)

- Decrease number of inputs
- Remove 3 code digits as inputs
 - Use code registers
 - Make them loadable from value
 - Need 3 load signal inputs (net gain in input $(4*3)-3=9$)
 - Could be done with 2 signals and decoder (ld1, ld2, ld3, load none)

